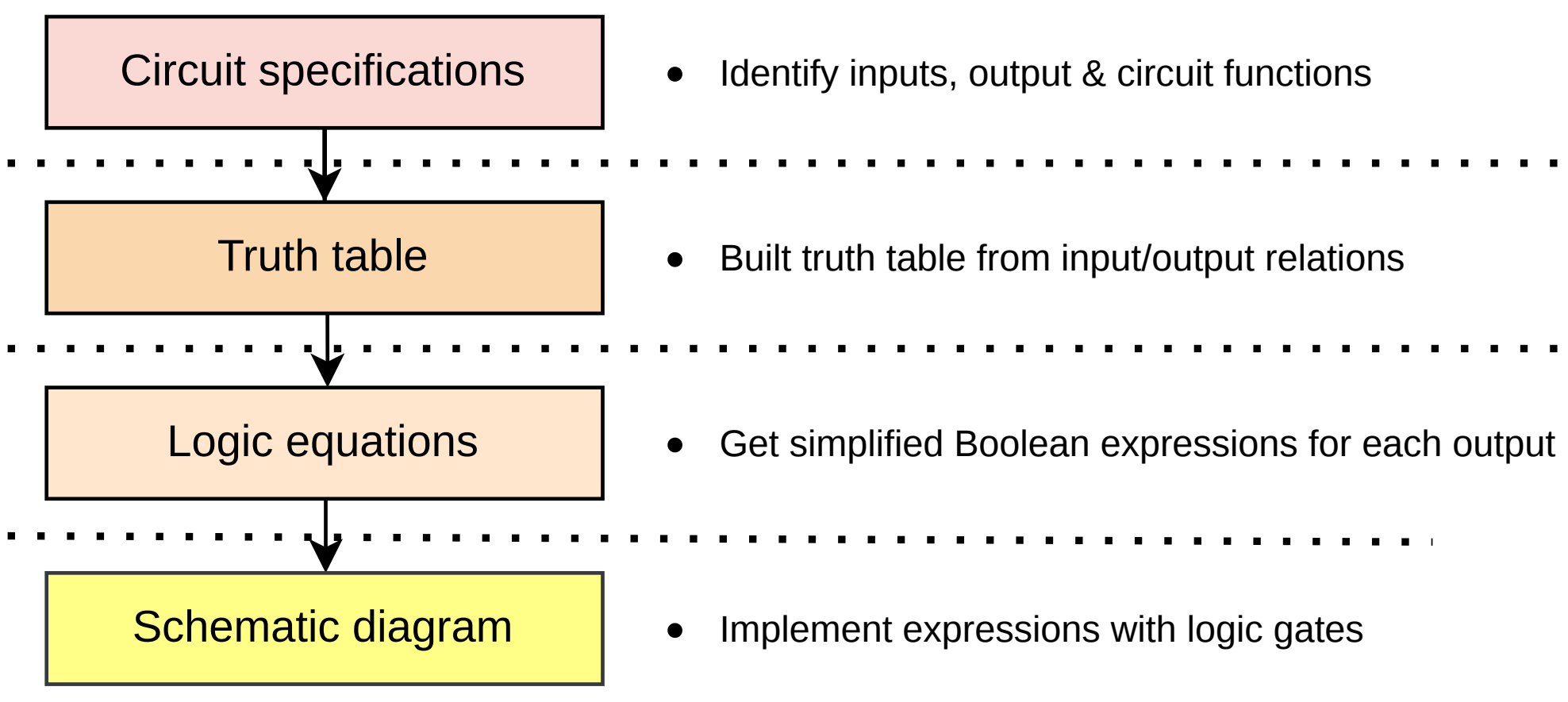
Circuit specifications
Identify inputs, output & circuit functions
Truth table
Built truth table from input/output relations
Logic equations
Get simplified Boolean expressions for each output
Schematic diagram
Implement expressions with logic gates