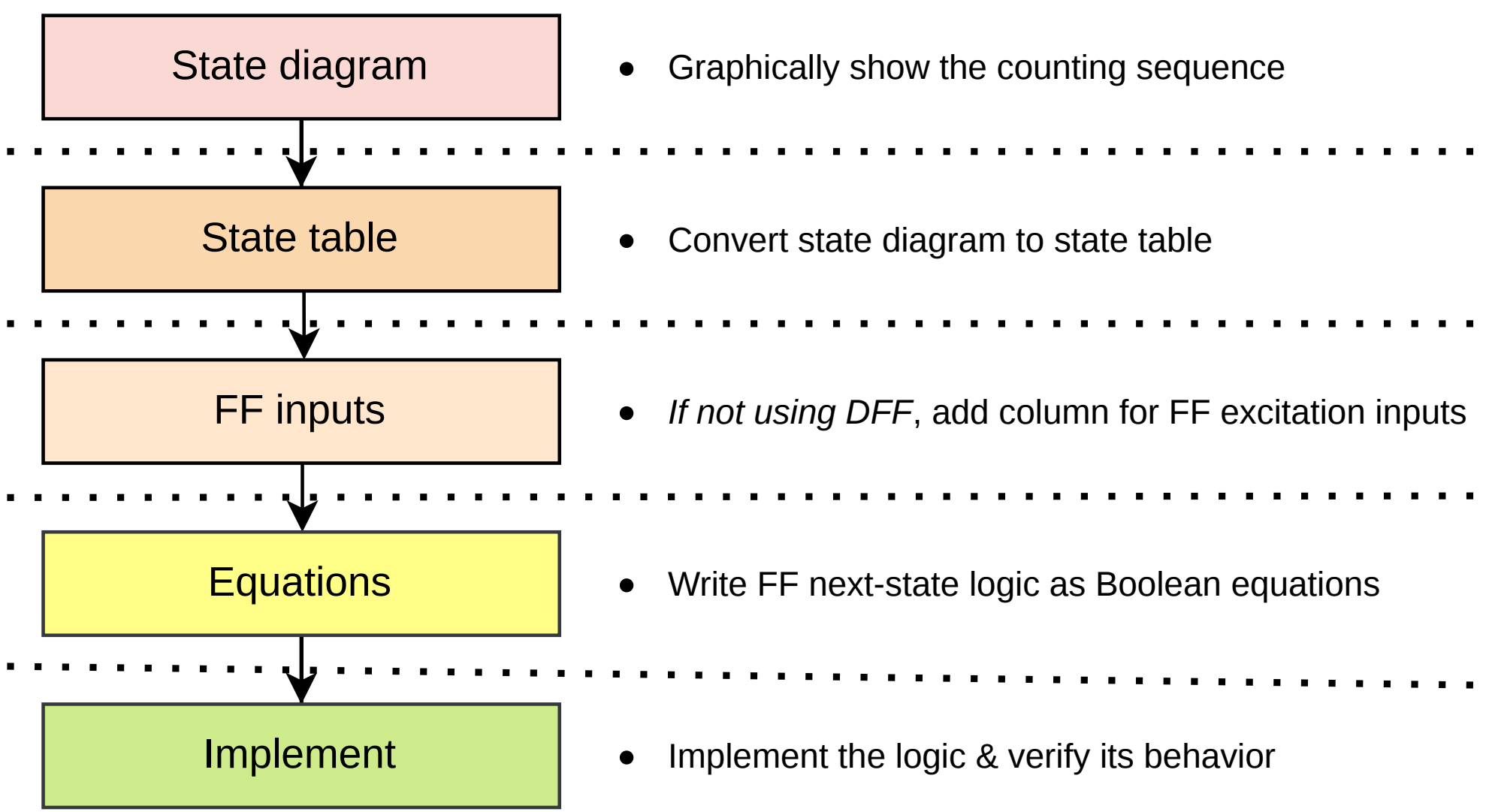
State diagram
Graphically show the counting sequence
State table
Convert state diagram to state table
FF inputs
If not using DFF, add column for FF excitation inputs
Equations
Write FF next-state logic as Boolean equations
Implement
Implement the logic & verify its behavior