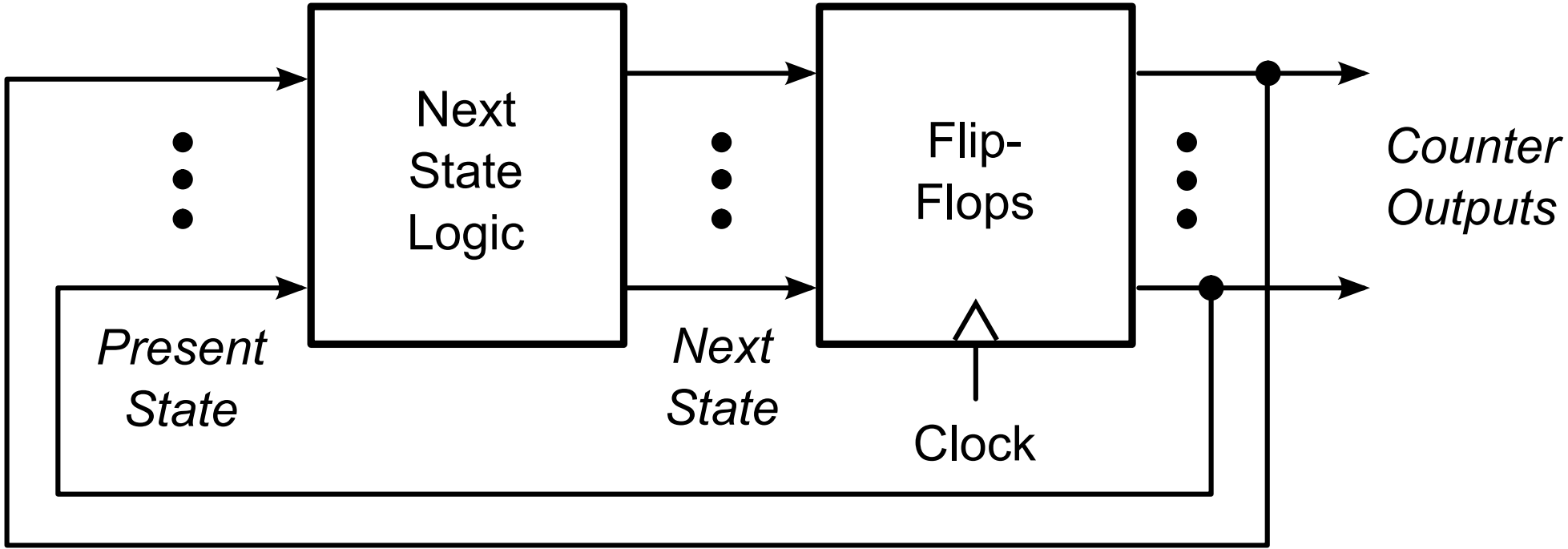
Next
State
Logic
Flip-
Flops
Counter
Outputs
Present
State
Next
State
Clock