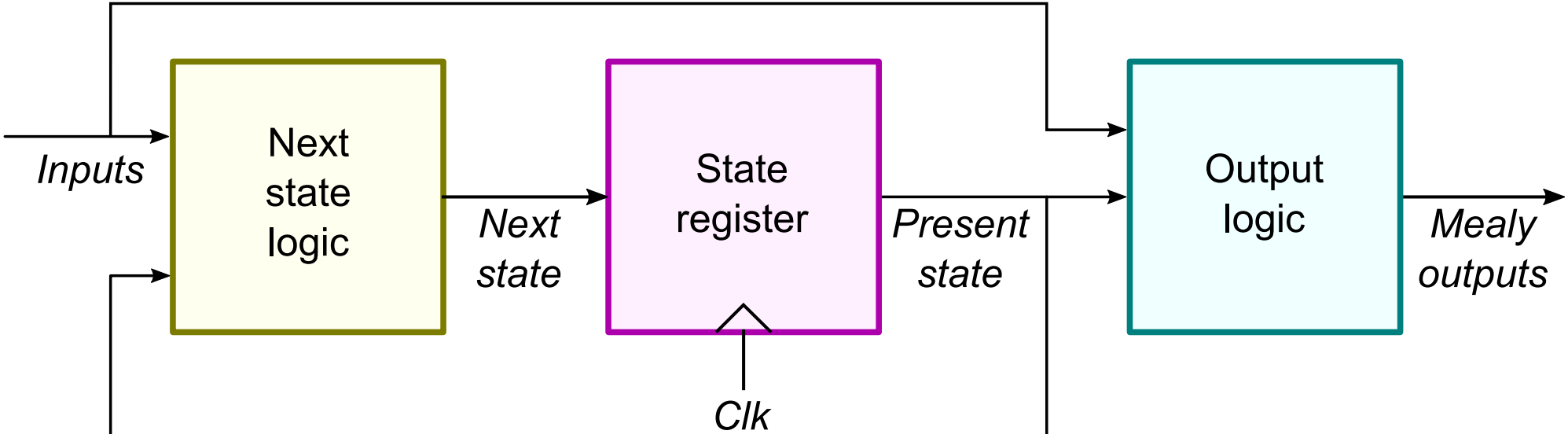
Inputs
Next state logic
Next state
State register
Present state
Output logic
Mealy outputs
Clk