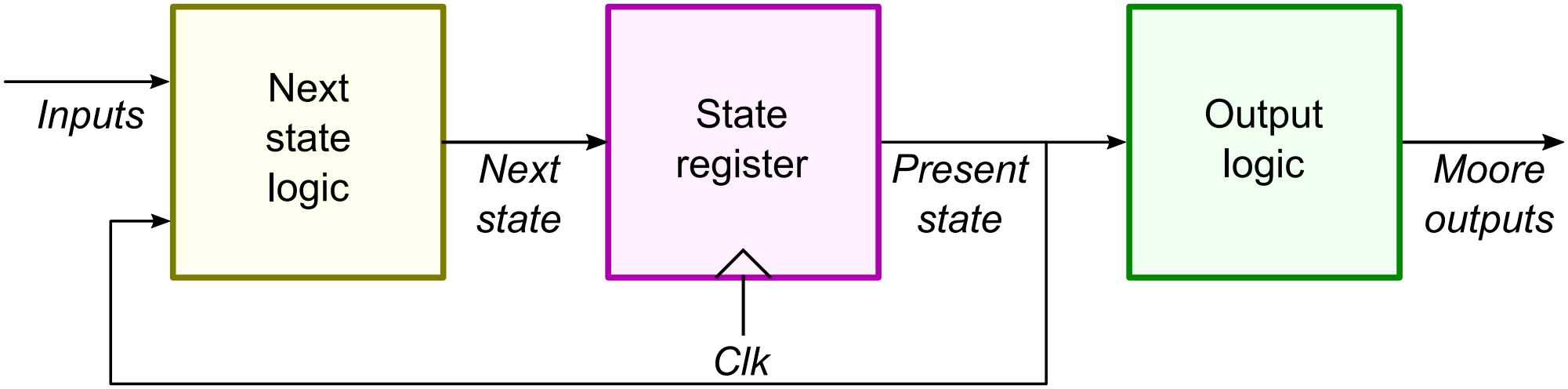
Inputs
Next state logic
Next state
State register
Present state
Output logic
Moore outputs
Clk