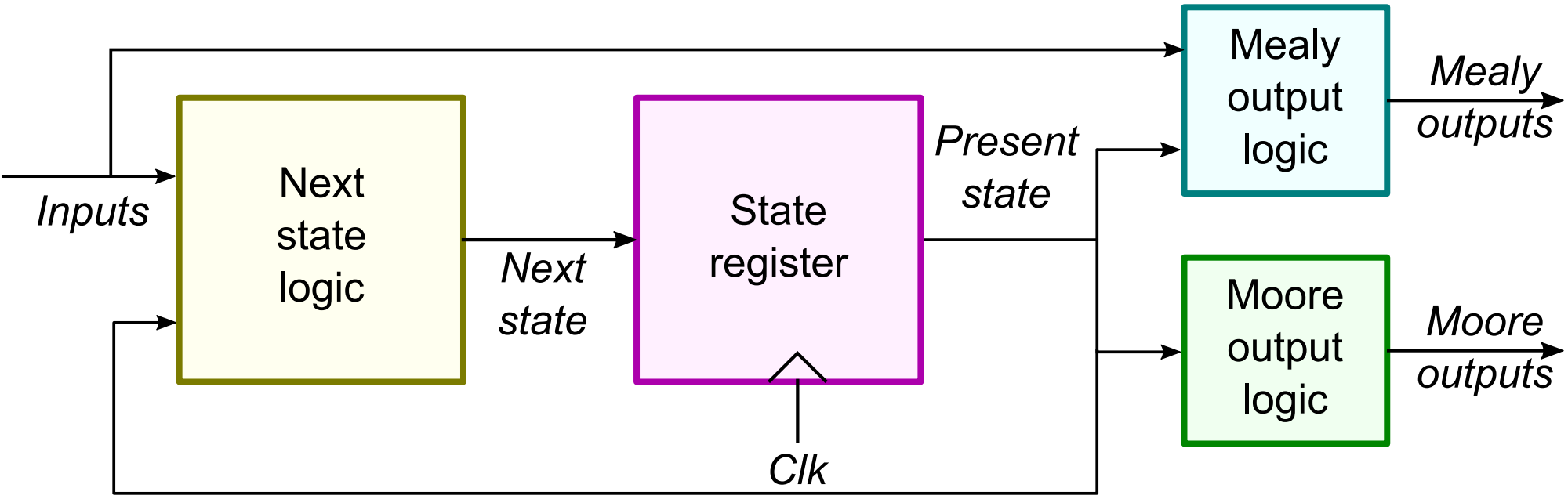
Inputs
Next state logic
Next state
State register
Present state
Clk
Mealy output logic
Mealy outputs
Moore output logic
Moore outputs