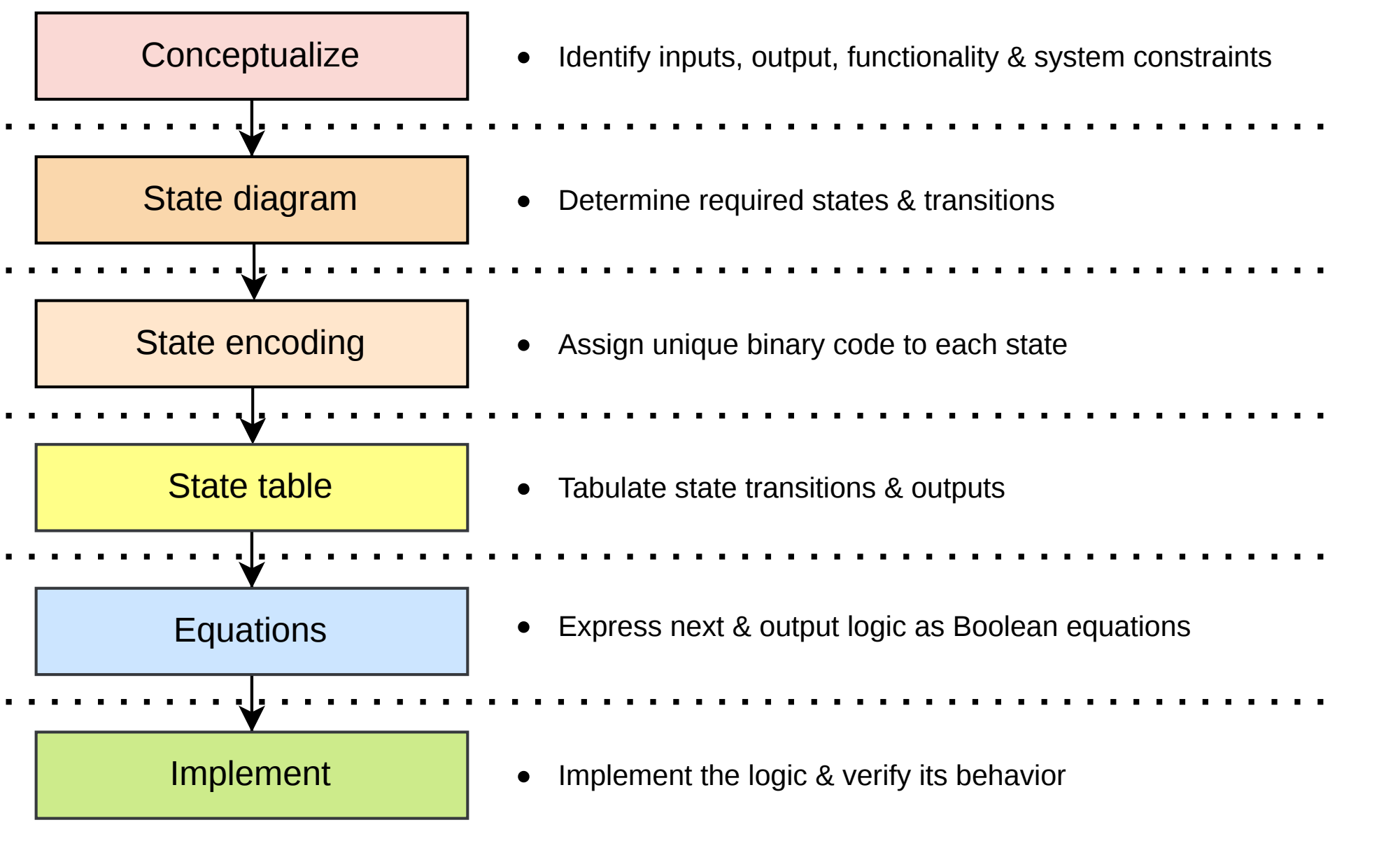
Conceptualize
Identify inputs, output, functionality & system constraints
State diagram
Determine required states & transitions
State encoding
Assign unique binary code to each state
State table
Tabulate state transitions & outputs
Equations
Express next & output logic as Boolean equations
Implement
Implement the logic & verify its behavior