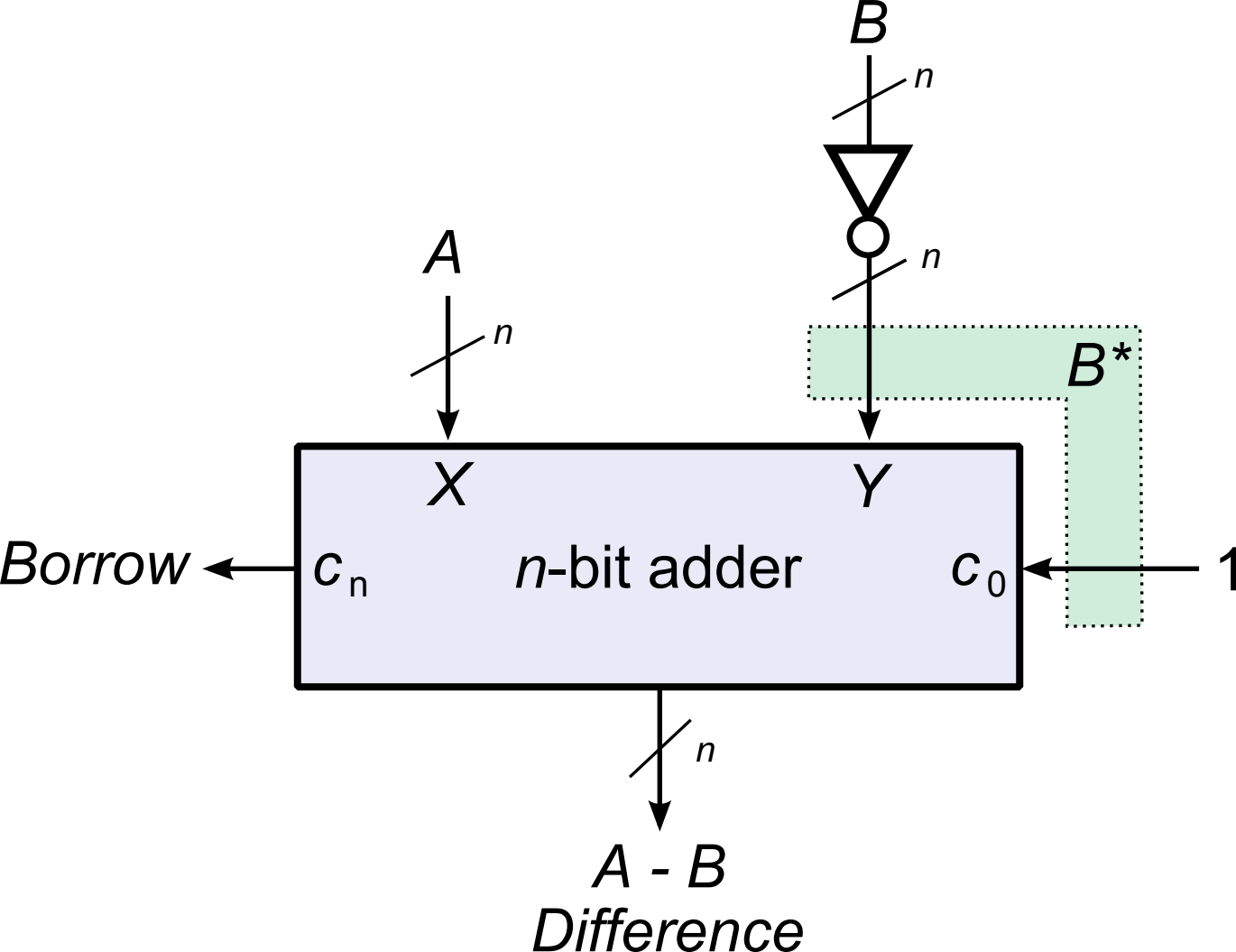
B
n
n
A
n
B*
X
Y
Borrow
c_n
n-bit adder
c_0
1
n
A - B
Difference