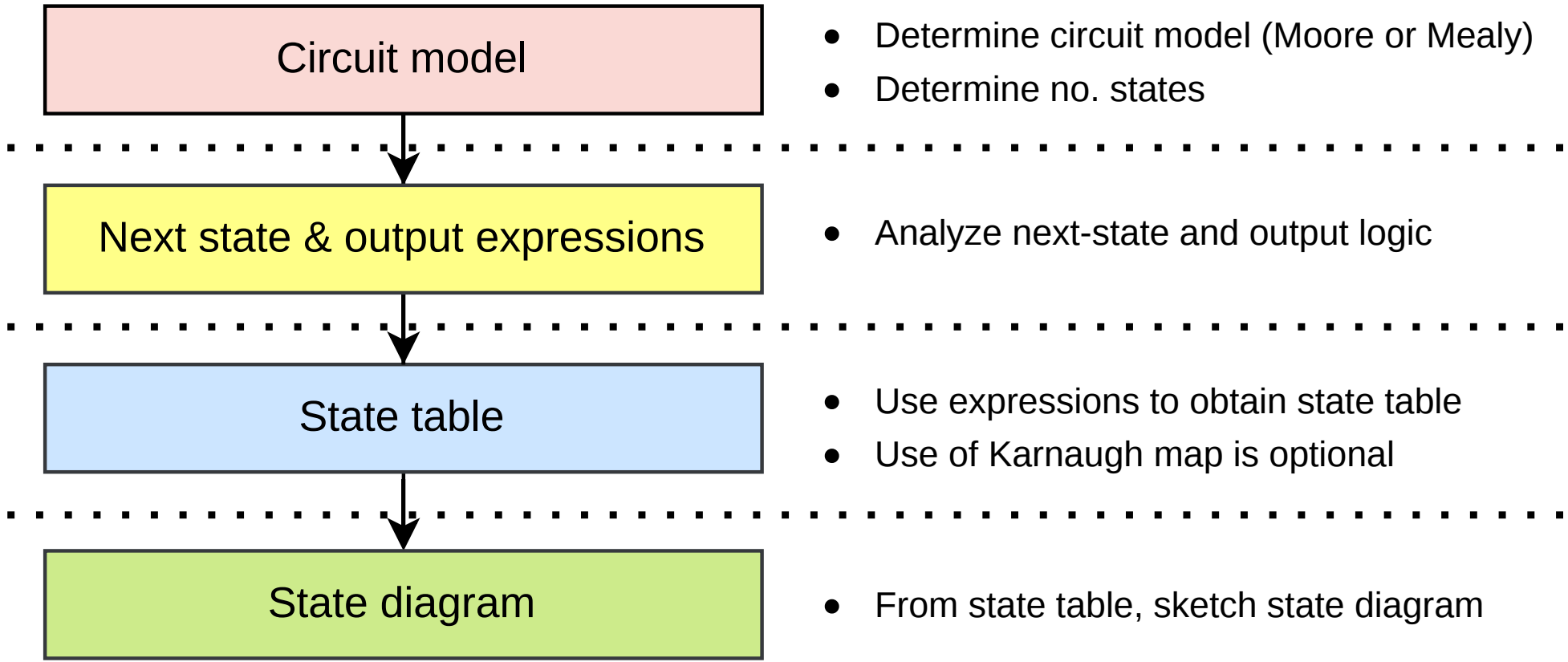
Circuit model
Next state & output expressions
State table
State diagram
Determine circuit model (Moore or Mealy)
Determine no. states
Analyze next-state and output logic
Use expressions to obtain state table
Use of Karnaugh map is optional
From state table, sketch state diagram